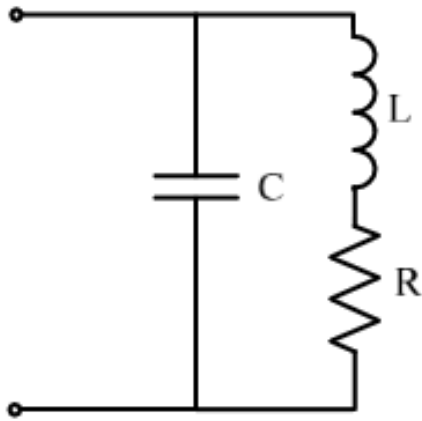


GATE 2022 EE 28

EE23BTECH11032 - Kaustubh Parag Khachane *

Question GATE 22 EE 28 :

The network shown below has a resonant frequency of 150 kHz and a bandwidth of 600 Hz. The Q -factor of the network is ____
(GATE EE 2022)



Solution:

In the state of resonance ,

Parameter	Description	Values
f_0	Resonant Frequency	
ω_0	Resonant angular frequency	$2\pi f_0$
R	Given resistance	
C	Given capacitance	
L	Given inductance	
V	Voltage applied	
I_0	Peak current	$\frac{V}{R}$

TABLE 0
PARAMETER TABLE

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (1)$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad (2)$$

Bandwidth is range of frequencies where power is \geq maximum power.

Hence it is the range of frequencies between the two points where power is half.

$$\text{Power is half} \Rightarrow I = \frac{I_0}{\sqrt{2}} \quad (3)$$

Current at any point is given by ,

$$\frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{V}{R\sqrt{2}} \quad (4)$$

Solving the above equation, we will get two solution ω_1 and ω_2 which will satisfy

$$\left(\omega L - \frac{1}{\omega C}\right) = \pm R \quad (5)$$

$$\Rightarrow \omega_2 - \omega_1 = \frac{R}{L} \quad (6)$$

$$\therefore \text{Bandwidth} = \frac{R}{L} \quad (7)$$

$$Q \text{ factor} = 2\pi \frac{\text{Peak energy stored}}{\text{Energy dissipated in one cycle}} \quad (8)$$

$$= \frac{\frac{1}{2}LI^2}{\frac{1}{2}I^2R\frac{1}{f_0}} \quad (9)$$

$$= \frac{\omega_0}{\frac{R}{L}} \quad (10)$$

$$(11)$$

Using equations (1) and (7),

$$Q = \frac{150000}{600} \quad (12)$$

$$= 250 \quad (13)$$